

## CS 20 Laboratory 1: Introduction to Electric Circuits


### 1. Resistor Color Bands

Label	Resistor Color Bands	Computed Resistance
R1	Brown, Orange, Brown, Gold	130 $\Omega$ , 5%
R2	Red, Red, Brown, Gold	220 $\Omega$ , 5%
R3	Green, Blue, Brown, Gold	560 $\Omega$ , 5%
R4	Brown, Red, Red, Gold	1200 $\Omega$ , 5%

### 2. Series Circuits

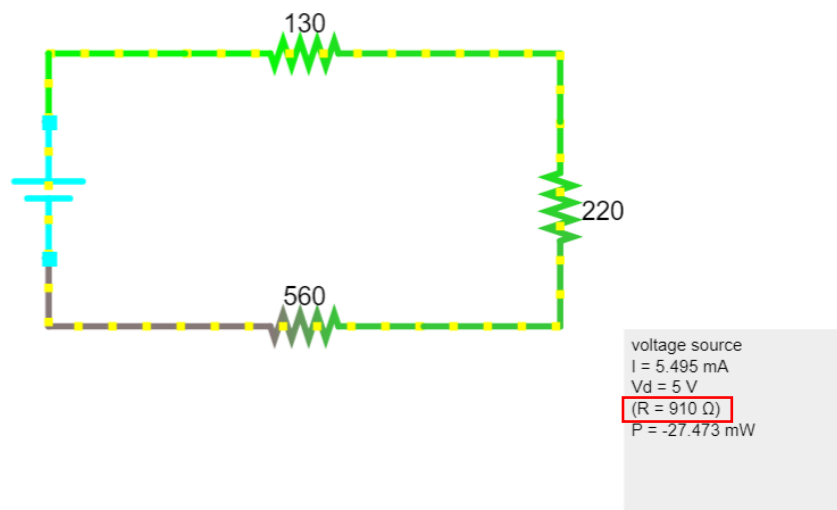(a) Since the circuit is in series,  $R_{eff} = R_1 + R_2 + \dots + R_n$


$$R_{eff} = R_1 + R_2 + R_3 = 130 \Omega + 220 \Omega + 560 \Omega = 910 \Omega$$



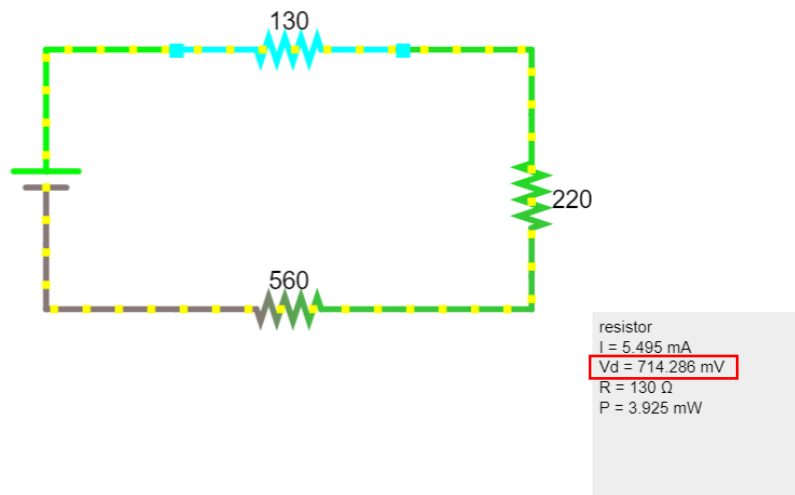(b) In the previous item, the resistance is given by  $R_{eff} = 910 \Omega$  and voltage is 5 V.


For  $V_1$ :

$$V_1 = \left( \frac{R_1}{R_{eff}} \right) (V) = \left( \frac{130 \Omega}{910 \Omega} \right) (5V) = 0.7142857143 V \approx 0.714 V \text{ or } 714.286 mV$$




For  $V_2$ :
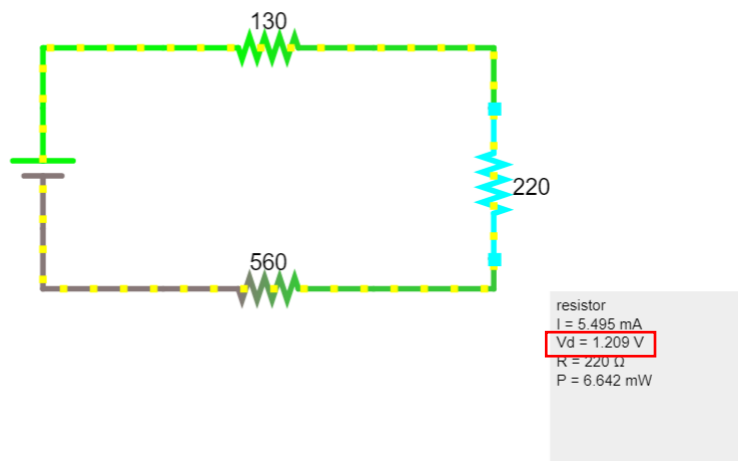
$$V_2 = \left( \frac{R_2}{R_{eff}} \right) (V) = \left( \frac{220 \Omega}{910 \Omega} \right) (5V) = 1.208791209 V \approx 1.209 V$$




For  $V_3$ :
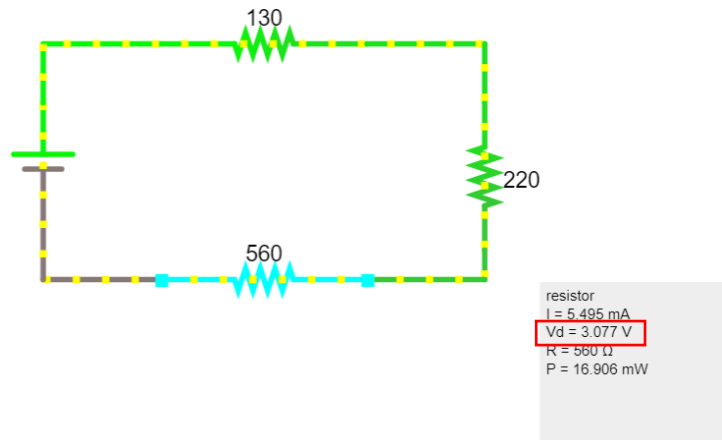
$$V_3 = \left( \frac{R_3}{R_{eff}} \right) (V) = \left( \frac{560 \Omega}{910 \Omega} \right) (5V) = 3.076923077 V \approx 3.077 V$$



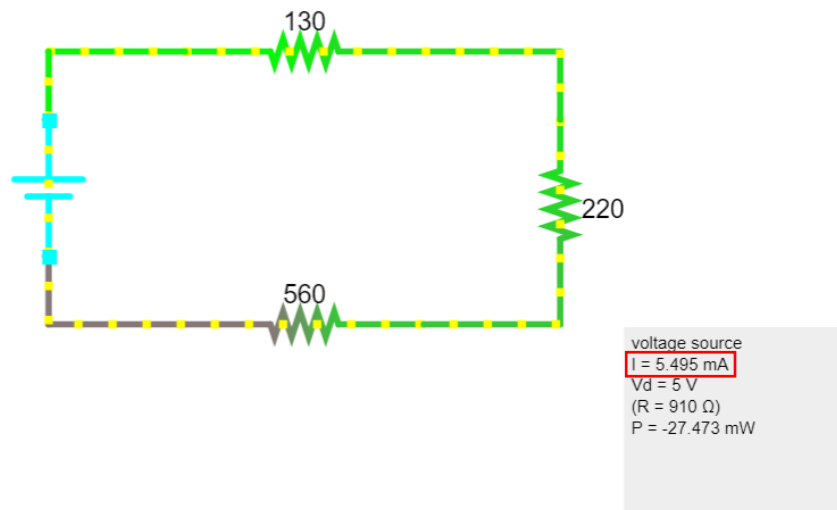(c) To compute for the theoretical current through the circuit, use Ohm's Law:

$$I = \frac{V}{R} = \frac{5\text{ V}}{910\ \Omega} = 5.49505495 \times 10^{-3}\text{ A} \approx 5.495\text{ mA}$$




### 3. Parallel Circuits

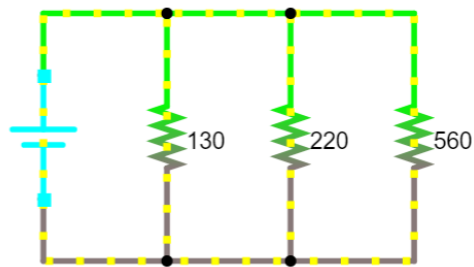(a) Since the circuit is in parallel,  $\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$

$$\frac{1}{R_{eff}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{130\ \Omega} + \frac{1}{220\ \Omega} + \frac{1}{560\ \Omega} = \frac{1123}{80080}\ \Omega$$

$$R_{eff} = \left( \frac{1}{R_{eff}} \right)^{-1} = \left( \frac{1123}{80080}\ \Omega \right)^{-1} = 71.30899377\ \Omega \approx 71.309\ \Omega$$



voltage source  
I = 70.117 mA  
Vd = 5 V  
**R = 71.309 Ω**  
P = -350.587 mW


(b) In the previous item, the resistance is given by  $R_{eff} \approx 71.309 \Omega$  and voltage is 5V.

To solve the theoretical current of each resistor, compute first for the current through the entire network:

$$\text{Using Ohm's Law, } I = \frac{V}{R} = \frac{5 \text{ V}}{71.309 \Omega} = 0.07011738262 \text{ A} \approx 0.07 \text{ A or } 70.117 \text{ mA}$$

For  $i_1$ :

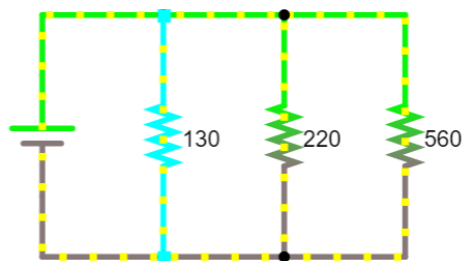
$$i_1 = \left( \frac{\frac{1}{R_1}}{\frac{1}{R_{eff}}} \right) (i) = \left( \frac{\frac{1}{130 \Omega}}{\frac{1}{71.309 \Omega}} \right) (0.07 \text{ A}) = 0.03846153846 \text{ A} \approx 0.0385 \text{ A or } 38.462 \text{ mA}$$



resistor  
**I = 38.462 mA**  
Vd = 5 V  
R = 130 Ω  
P = 192.308 mW

For  $i_2$ :

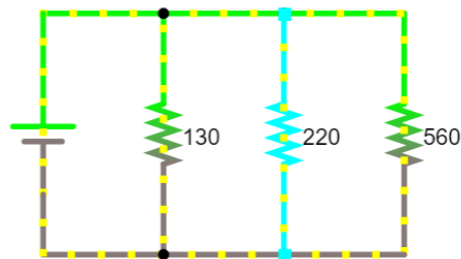
$$i_2 = \left( \frac{\frac{1}{R_2}}{\frac{1}{R_{eff}}} \right) (i) = \left( \frac{\frac{1}{220 \Omega}}{\frac{1}{71.309 \Omega}} \right) (0.07 A) = 0.02272727273 A \approx 0.0227 A \text{ or } 22.727 \text{ mA}$$



resistor  
I = 22.727 mA  
Vd = 5 V  
R = 220  $\Omega$   
P = 113.636 mW

For  $i_3$ :

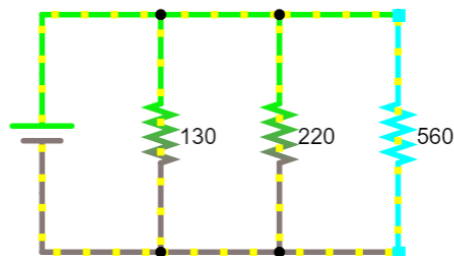
$$i_3 = \left( \frac{\frac{1}{R_3}}{\frac{1}{R_{eff}}} \right) (i) = \left( \frac{\frac{1}{560 \Omega}}{\frac{1}{71.309 \Omega}} \right) (0.07 A) = 8.928571429 \times 10^{-3} A \approx 8.929 \text{ mA}$$



resistor  
I = 8.929 mA  
Vd = 5 V  
R = 560  $\Omega$   
P = 44.643 mW

(c) To compute for the theoretical voltage through the circuit, use Ohm's Law:

$$V = IR = (0.07A)(71.309 \Omega) = 5V$$

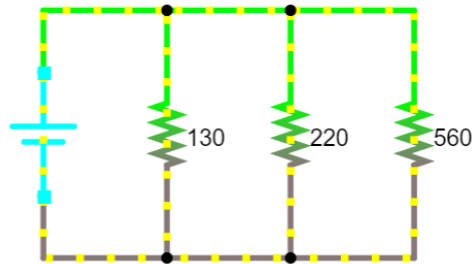

voltage source  
I = 70.117 mA  
**Vd = 5 V**  
(R = 71.309  $\Omega$ )  
P = -350.587 mW