


## CS 20 Laboratory 10: Read Only Memory

### 1. (4 pts) Basics

- a. (2pts) For items 10-13 of Section 2.1, answer the question, include pictures of the circuit with the inputs and LED outputs (we expect 4), and attach the Logisim file (cs20lab10\_1a.circ) of the circuit. Make sure that the circuit is well labelled on which is A4, A3, etc. and O7, O6, etc.

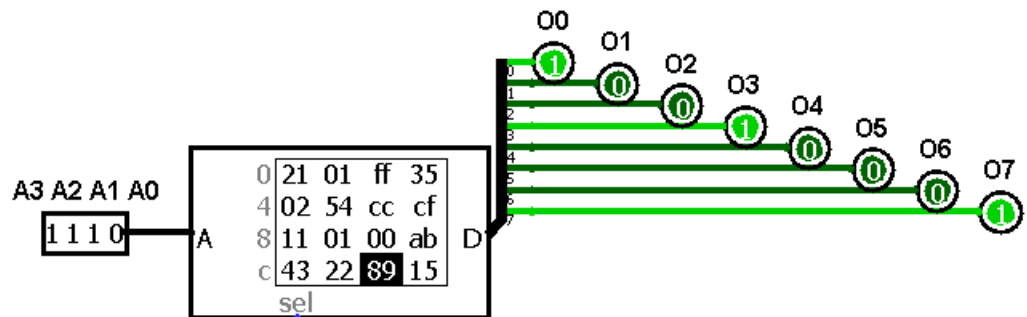
10) To access the cell containing the value 89, what should the input pins be? What pattern did you observe in the output LEDs?

The input pins should be 1110, while the output LEDs are 10001001 (with O7 as the MSB and O0 as the LSB) which is the binary equivalent of  $89_{16}$ .



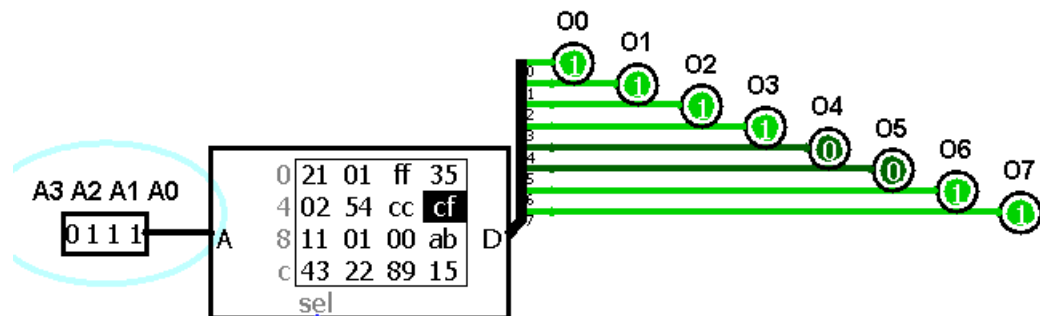
11) To access the cell containing the value cf, what should the input pins be? What pattern did you observe in the output LEDs?

The input pins should be 0111, while the output LEDs are 11001111 (with O7 as the MSB and O0 as the LSB) which is the binary equivalent of  $cf_{16}$ .



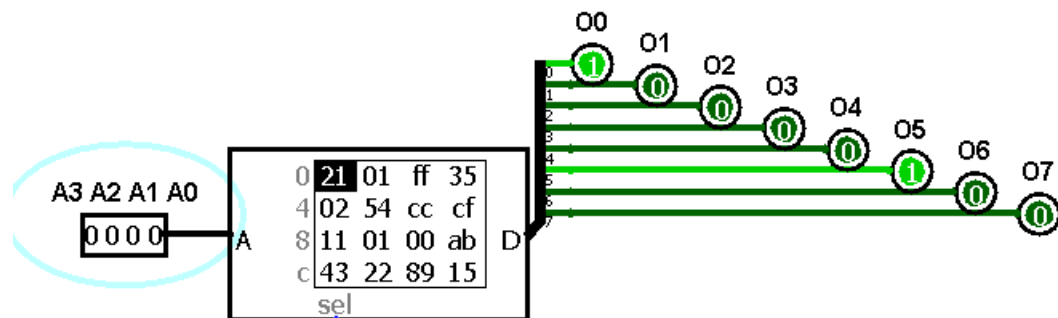
12) To access the cell containing the value 21, what should the input pins be? What pattern did you observe in the output LEDs?

The input pins should be 0000, while the output LEDs are 00100001 (with O7 as the MSB and O0 as the LSB) which is the binary equivalent of  $21_{16}$ .



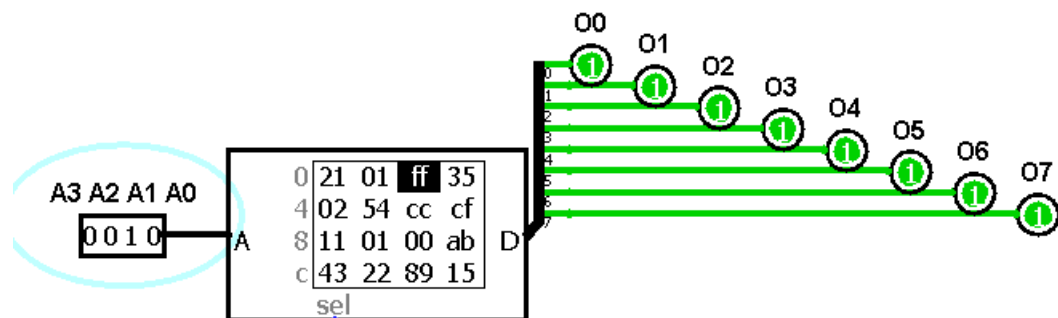
13) To access the cell containing the value ff, what should the input pins be? What pattern did you observe in the output LEDs?

The input pins should be 0010, while the output LEDs are 11111111 (with O7 as the MSB and O0 as the LSB) which is the binary equivalent of  $ff_{16}$ .



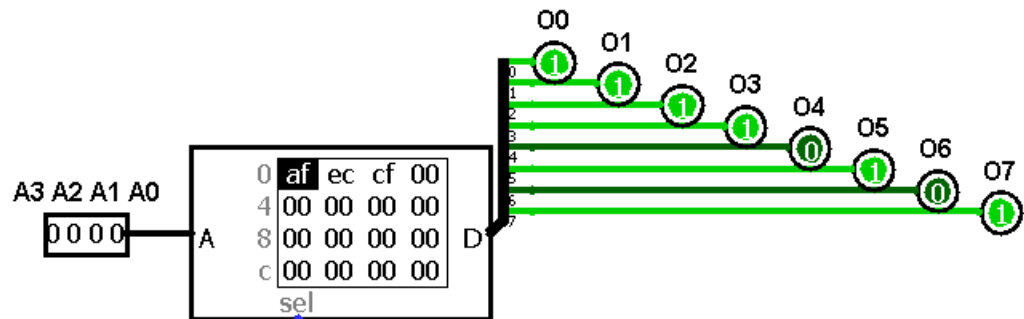
- b. (1pt) For item 14 of Section 2.1, explain how you met the requirement – what cells or entries in the ROM needed to be programmed, and to what values. Include a picture of the circuit and attach the Logisim file (cs20lab10\_1b.circ) of the circuit.

The word 0xCFECAf is made up of 24 bits. To store it in the ROM, only 3 cells were used since 1 cell is equivalent to a byte or 8 bits ( $3 \times 8 = 24$ ). Since the word is in little endian, the LSB will be in the lowest numbered byte followed by the next bits. Hence, address 0000 contains 0xaf, address 0001 contains 0xec, and address 0010 contains 0xcf.






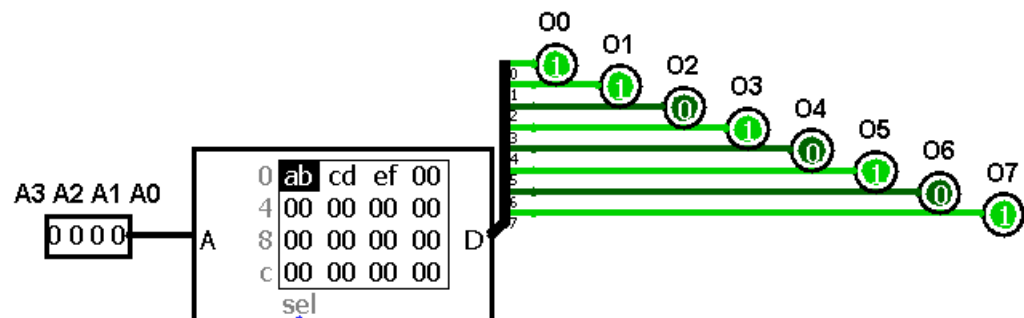
- c. (1pt) For item 15 of Section 2.1, explain how you met the requirement – what cells or entries in the ROM needed to be programmed, and to what values. Include a picture of the circuit and attach the Logisim file (cs20lab10\_1c.circ) of the circuit.

The word 0xABCDEF is made up of 24 bits. To store it in the ROM, only 3 cells were used since 1 cell is equivalent to a byte or 8 bits ( $3 \times 8 = 24$ ). Since the word is in big endian, the MSB will be in the lowest numbered byte followed by the next bits. Hence, address 0000 contains 0xab, address 0001 contains 0xcd, and address 0010 contains 0xef.



## 2. (2pts) Logic gates using memory (look-up table)

 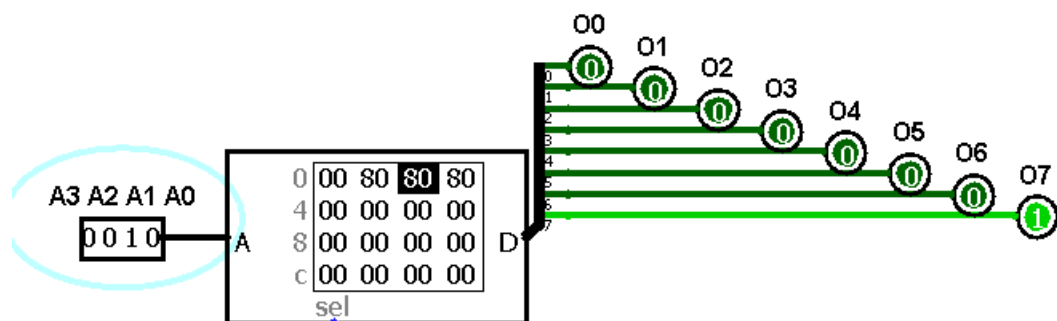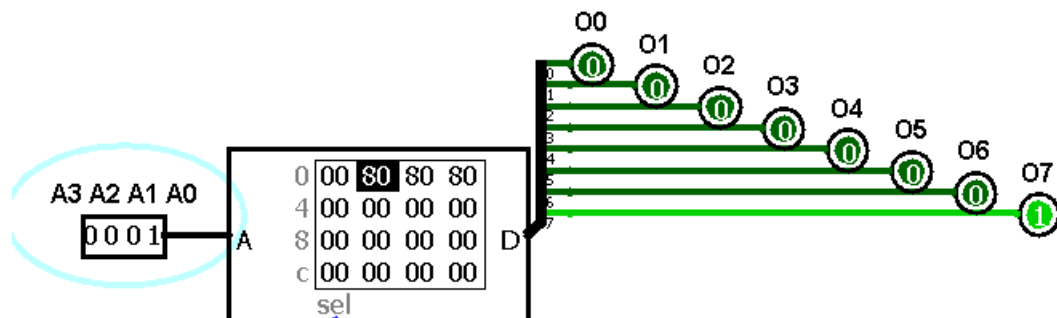 - a. (2pts) For Section 2.2, include pictures showing/proving that the ROM chip indeed acts as a 2-input OR gate. We expect 4 pictures in total - make sure that these pictures/ are well-labelled. Attach also the labelled Logisim file (cs20lab10\_2.circ) of the circuit.



### 3. (4pts) Complex logic functions using memory (look-up table)

- a. (2pts) Explain how you met the requirement in Section 2.3 - what cells or entries in the ROM needed to be programmed, and to what values. For each ROM entry edited, explain its programmed content in relation to the BCD output representing the product of the two inputs, input1 and input2.

In order to visualize the 2-bit multiplier, I created a table with corresponding decimal and hexadecimal equivalents.

Input 1		Input 2		Decimal Output	Output				Reversed Output	Hexadecimal equivalent
A3	A2	A1	A0		O0	O1	O2	O3		
0	0	0	0	0	0	0	0	0	0000	0
0	0	0	1	0	0	0	0	0	0000	0
0	0	1	0	0	0	0	0	0	0000	0
0	0	1	1	0	0	0	0	0	0000	0
0	1	0	0	0	0	0	0	0	0000	0
0	1	0	1	1	0	0	0	1	1000	8
0	1	1	0	2	0	0	1	0	0100	4
0	1	1	1	3	0	0	1	1	1100	C
1	0	0	0	0	0	0	0	0	0000	0
1	0	0	1	2	0	0	1	0	0100	4
1	0	1	0	4	0	1	0	0	0010	2
1	0	1	1	6	0	1	1	0	0110	6
1	1	0	0	0	0	0	0	0	0000	0
1	1	0	1	3	0	0	1	1	1100	C
1	1	1	0	6	0	1	1	0	0110	6
1	1	1	1	9	1	0	0	1	1001	9

For addresses 0000, 0001, 0010, 0100, 1000, and 1100 – since there is a 00 input, their product should be 0 hence, their values would also be 00.

As for address 0101 which represents  $01_2 * 01_2$ , the answer should be  $0001_2$  ( $1_{10}$ ). However, 00 acts as the MSB of the decoder, so the input of the decoder would be reverse the output (until O3) of the ROM. Hence, instead of  $0001_2$ , the value of the ROM will become  $1000_2$  which is  $0x08$ .

The same thought process is done with the non-zero products. For address 0110 which represents  $01_2 * 10_2 = 0010_2$  ( $2_{10}$ ), the reverse would be  $0100_2$  which is  $0x04$ .

For address 0111 which represents  $01_2 * 11_2 = 0011_2$  ( $3_{10}$ ), the reverse would be  $1100_2$  which is  $0x0c$ .

For address 1001 which represents  $10_2 * 01_2 = 0010_2$  ( $2_{10}$ ), the reverse would be  $0100_2$  which is  $0x04$ .

For address 1010 which represents  $10_2 * 10_2 = 0100_2$  ( $4_{10}$ ), the reverse would be  $0010_2$  which is  $0x02$ .

For address 1011 which represents  $10_2 * 11_2 = 0110_2$  ( $6_{10}$ ), the reverse would still be  $0110_2$  which is  $0x06$ .

For address 1101 which represents  $11_2 * 01_2 = 0011_2$  ( $3_{10}$ ), the reverse would be  $1100_2$  which is  $0x0c$ .

For address 1110 which represents  $11_2 * 10_2 = 0110_2$  ( $6_{10}$ ), the reverse would still be  $0110_2$  which is  $0x06$ .

Finally, for address 1111 which represents  $11_2 * 11_2 = 1001_2$  ( $9_{10}$ ), the reverse would still be  $1001_2$  which is  $0x09$ .

- b. (2pts) For Section 2.3, include pictures showing/proving that the ROM chip indeed acts as a 2-bit multiplier. We expect 16 pictures in total - make sure that these pictures are well-labelled (what was the input at that state, etc.). Attach also the labelled Logisim file (cs20lab10\_3.circ) of the circuit.

